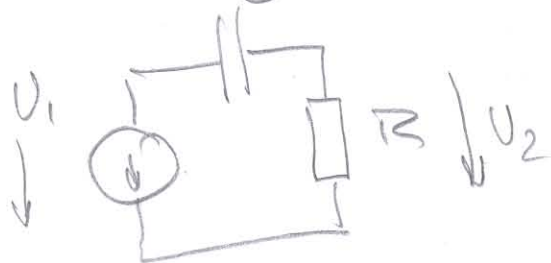


$$a) R_{vst} = h_{11b} \parallel R_4$$

$$R_{vst} = R_3 \parallel \frac{1}{h_{22}} \approx R_3$$

⊕ Vypočet hodnoty kondenzátoru
pre pokles o 3dB

V kóde kde nastane pokles o 3dB
určíme pre obvod



$$\frac{U_2}{U_1} = \frac{R}{R + \frac{1}{j\omega C}} ; \left| \frac{U_2}{U_1} \right| = \frac{\omega RC}{\sqrt{(\omega RC)^2 + 1}} =$$

$$n_{dB} = 20 \log \left| \frac{U_2}{U_1} \right| \Rightarrow \omega \rightarrow \infty \Rightarrow \left| \frac{U_2}{U_1} \right| = 1 \Rightarrow n' = 20 \log 1 = 0$$

$$\omega = ? \quad n' = -3 \text{ dB} = 20 \log \frac{1}{\sqrt{2}} = 20 \log 0,707$$

$$\text{Ak v menovateľni } \sqrt{2} \Rightarrow (\omega RC)^2 = 1$$

$$\Rightarrow \omega = \frac{1}{RC}$$

$$G_1 = \frac{1}{\omega R_{vst}} ; G_3 = \frac{1}{\omega(R_3 + R_L)} ; G_2 = \frac{1}{\omega(R_4 \parallel R_e)}$$